



COMPUTER ARCHITECTURE LAB2

FCIS Ainsams University
Spring2021

AGENDA

- N-bit Adder/Subtractor
- Generic Building Blocks of MIPS:
 - Sign extender
 - 32-bit ALU (Hands-on 1)

SIGN EXTENDER

Sign extension is the operation, in computer arithmetic, of increasing the number of bits of a binary number while preserving the number's sign (positive/negative) and value.

In (4)	Out(8)
1010	11111010
0101	00000101

Out = “0000” & IN = X“0” & IN

Out = “1111” & IN = X“f” & IN

SIGN EXTENDER

Library **IEEE**;

USE **IEEE.STD_LOGIC_1164.ALL**;

ENTITY signext IS — sign extender

PORT (a : IN **STD_LOGIC_VECTOR**(15 DOWNT0 0);

 y : **OUT STD_LOGIC_VECTOR**(31 DOWNT0 0));

END;

ARCHITECTURE beave **OF** signext IS

BEGIN


 y <= X"ffff" & a WHEN a(15) = '1' ELSE

 X"0000" & a;

END beave;



4-BIT PARALLEL ADDER (1)

 

4-BIT PARALLEL ADDER (2)

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
ENTITY adder IS
```

```
PORT ( A: IN STD_LOGIC_VECTOR (3 DOWNTO 0);
```

```
       B: IN STD_LOGIC_VECTOR (3 DOWNTO 0);
```

```
       S: OUT STD_LOGIC_VECTOR (3 DOWNTO 0);
```

```
       Carry : OUT STD_LOGIC);
```

```
END adder;
```

-- Q2) but what about carry??

```
ARCHITECTURE Behavioral OF adder IS
```

```
BEGIN
```


```
    S <= A + B;
```

```
END Behavioral;
```

Q1) Is the synthesizer inferred an 4-bit adder ?

4-BIT PARALLEL ADDER (3)

- ADDER RTL

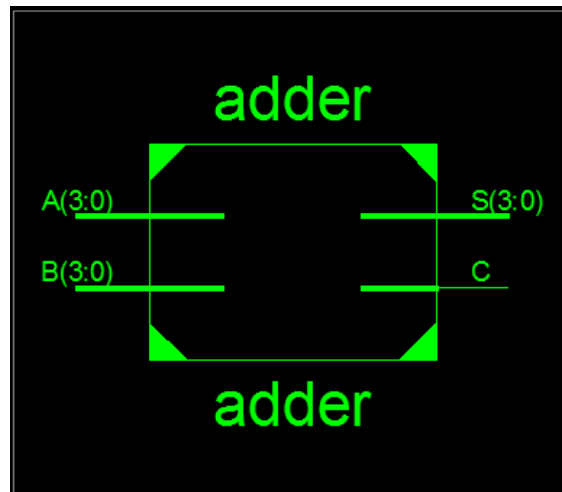

- Part of Synthesizer report

```
-----*-----
                        HDL Synthesis
-----*-----

Synthesizing Unit <adder>.
  Related source file is "c:/users/amahany/desktop/test/archi2/lab2/adder.vhd".
  Found 4-bit adder for signal <S> created at line 44.
  Summary.
  [ inferred 1 Adder/Subtractor(s). ]
Unit <adder> synthesized.
```

A1) YES it's inferred as Adder

4-BIT PARALLEL ADDER (4) -CARRY

```
ENTITY adder IS PORT (  
  A: IN      STD_LOGIC_VECTOR      (3 DOWNTO 0);  
  B: IN      STD_LOGIC_VECTOR      (3 DOWNTO 0);  
  S: OUT     STD_LOGIC_VECTOR      (3 DOWNTO 0);  
  Cin : IN   STD_LOGIC;  
  Carry : OUT STD_LOGIC);
```

```
END adder;
```

```
ARCHITECTURE Behavioral OF adder IS
```

```
  SIGNAL Tmp: STD_LOGIC_VECTOR (4 DOWNTO 0);
```

```
  BEGIN
```

```
    Tmp <= ('0' & A) + ('0' & B)+Cin;
```

```
    S <= Tmp(3 DOWNTO 0);
```

```
    Carry <= Tmp(4);
```

```
  END Behavioral;
```


4-BIT PARALLEL ADDER (4) -CARRY

```
ENTITY adder IS PORT (  
  A: IN      STD_LOGIC  
  B: IN      STD_LOGIC  
  S: OUT     STD_LOGIC  
  Cin : IN   STD_LOGIC;  
  Carry : OUT STD_LOGIC  
END adder;  
ARCHITECTURE Behavioral  
  SIGNAL Tmp: STD_LOGIC  
  BEGIN  
    Tmp <= ('0' & A) + ('0' &  
    S <= Tmp(3 DOWNTO  
    Carry <= Tmp(4);  
END Behavioral;
```

Q3) What if we want to implement parallel subtractor?

$\text{Tmp} \leq ('0' \& A) + ('0' \& B') + 1;$

Q4) What if we want to implement parallel adder/ subtractor?

$\text{Tmp} \leq ('0' \& A) + ('0' \& BB) + \text{Cin};$


1. Cin is 0 when add, 1 when sub
2. BB = B when Cin=0
B' when Cin =1

N-BIT ALU

- An Arithmetic/Logical Unit (ALU) combines a variety of mathematical and logical operations.
- ALU might perform addition, subtraction, magnitude comparison, AND, and OR operations.
- The ALU forms the heart of most computer systems.


N-BIT ALU

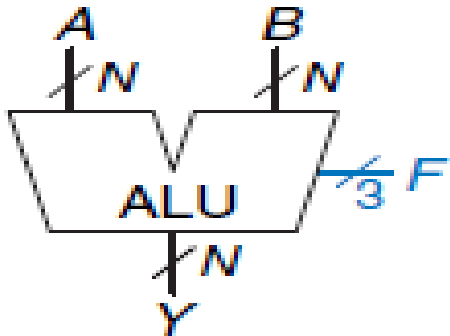- The ALU receives a control signal F that specifies which function to perform.
- A and B is input Signal.
- Y is output signal



$F_{2:0}$	Function
000	A AND B
001	A OR B
010	A + B
011	not used
100	A AND \bar{B}
101	A OR \bar{B}
110	A - B
111	SLT

HANDS-ON 1: 32-BIT ALU

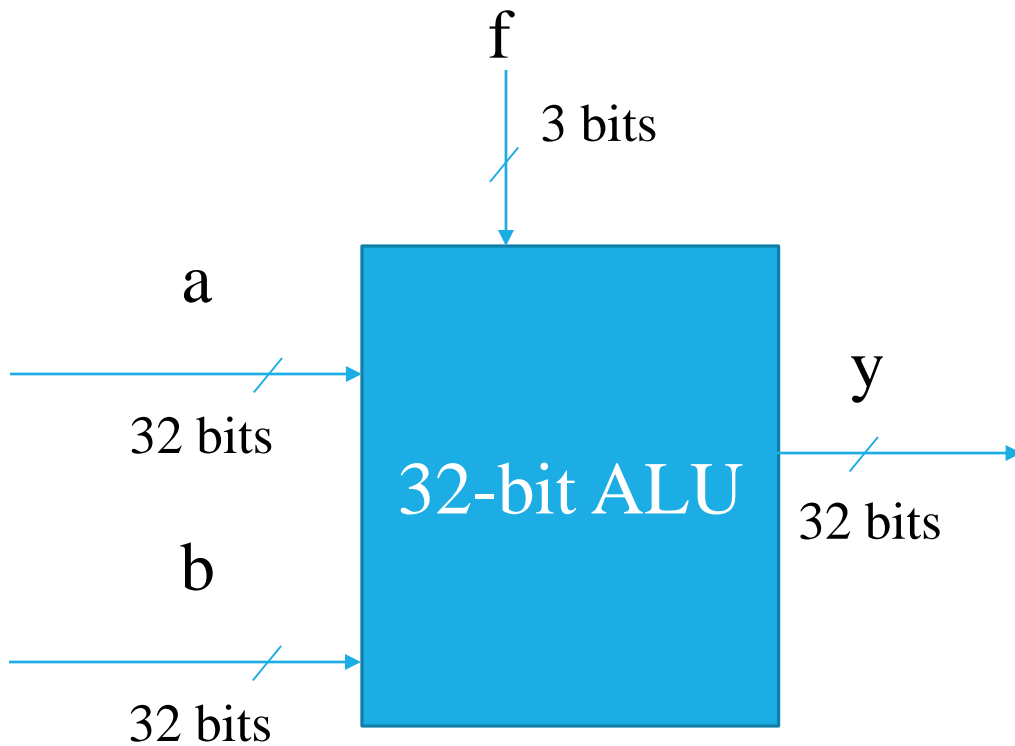

$F_{2:0}$	Function
000	A AND B
001	A OR B
010	A + B
011	not used
100	A AND \bar{B}
101	A OR \bar{B}
110	A - B
111	SLT

HANDS-ON 1: 32-BIT ALU

entity alu32 is

port(A, B: in STD_LOGIC_VECTOR(31 downto 0);

F: in STD_LOGIC_VECTOR(2 downto 0);

Y: out STD_LOGIC_VECTOR(31 downto 0));

end;

architecture synth of alu32 is

signal S, BB: STD_LOGIC_VECTOR(31 downto 0);

begin

BB <= (not B) when (F(2) = '1') else B;

S <= A + Bout + F(2);

Y <= A and Bout when F(1 downto 0) = "00" ELSE

A or Bout when F(1 downto 0) = "01" ELSE

S when F(1 downto 0) = "10" ELSE


("00000000000000000000000000000000" & S(31)) when F(1 downto 0) = "11"

ELSE X"00000000";

End synth;

HANDS-ON 1: 32-BIT ALU

ALU RTL

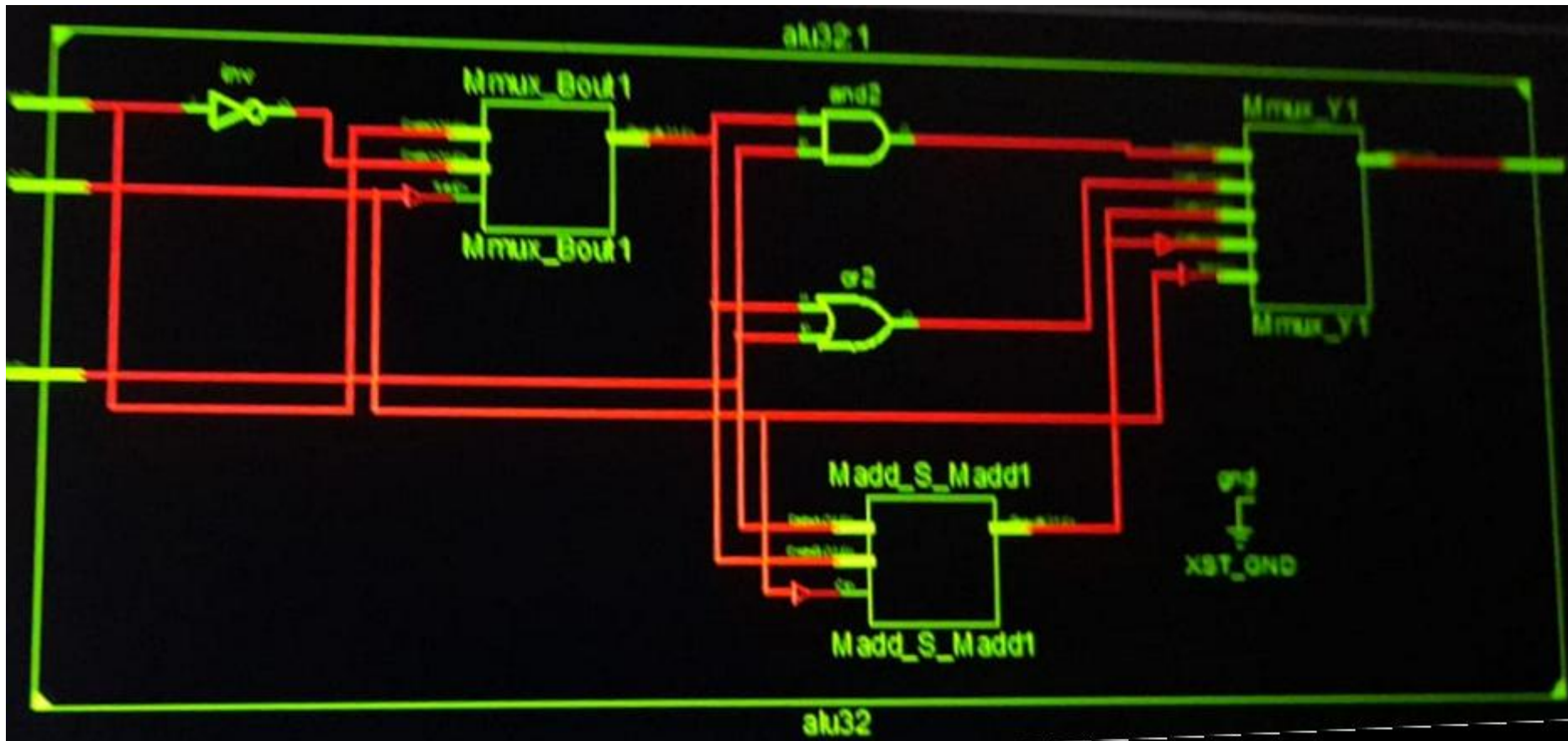



Thanks